




# **BCT 2205 – Lecture 3.2**

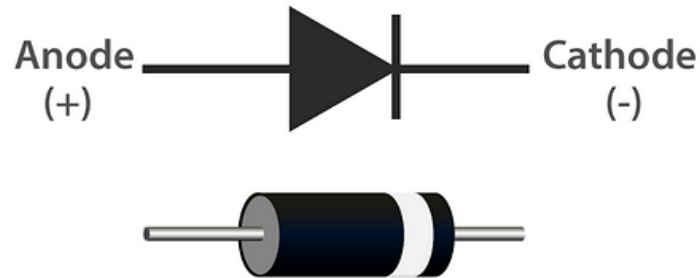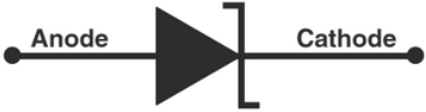

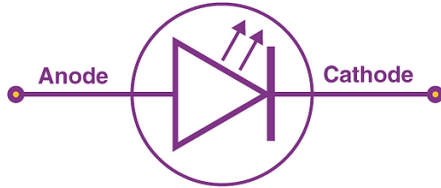

- **Semiconductor diodes and Transistors**

By J. Mathenge

# Semiconductor Diodes


- When a junction is formed between p-type and n-type semiconductor materials, the resulting device is called a **semiconductor diode**.
- A diode offers no resistance to current flow in one direction and an extremely high resistance to current flow in the other.
- Diodes are used in applications that require a circuit to behave differently according to the direction of current flowing in it.
- The connection to the **p-type** material is referred to as the **anode** while that to the **n-type** material is called the **cathode**.




<i>Zener diodes</i>	<i>Varactor diodes</i>	<i>Light emitting diodes (LED)</i>	<i>Schottky diodes</i>
<ul style="list-style-type: none"> <li>Heavily doped silicon diodes which exhibit an abrupt reverse break-down at relatively low voltages.</li> </ul> 	<ul style="list-style-type: none"> <li>Varying the width of the depletion region is equivalent to varying the plate separation of a very small capacitor.</li> </ul> 	<ul style="list-style-type: none"> <li>General-purpose indicators which operate from smaller voltages and currents.</li> <li>LEDs are reliable than filament lamps.</li> </ul> 	<ul style="list-style-type: none"> <li>Uses a metal-semiconductor contact rather than a p-n junction.</li> <li>Used to construct integrated circuits</li> </ul> 
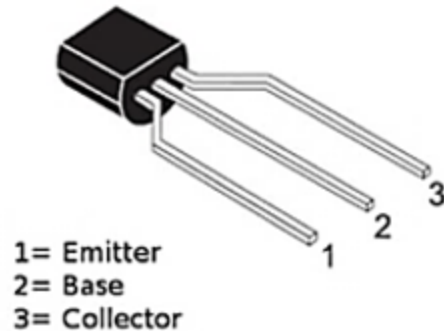
# Transistors


- The transistor is composed of a semiconductor material with three terminals for connection to an electronic circuit.
- Voltage or current applied to one pair of the transistor terminals controls the current through another pair of terminals.
- Bipolar transistors generally comprise n-p-n or p-n-p junctions of either silicon (Si) or germanium (Ge) material.



Typical transistor

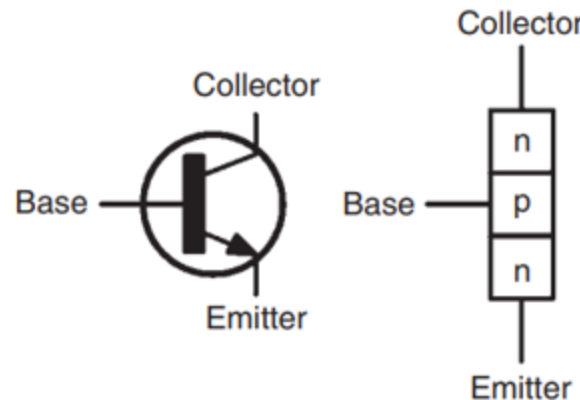



n-p-n transistor

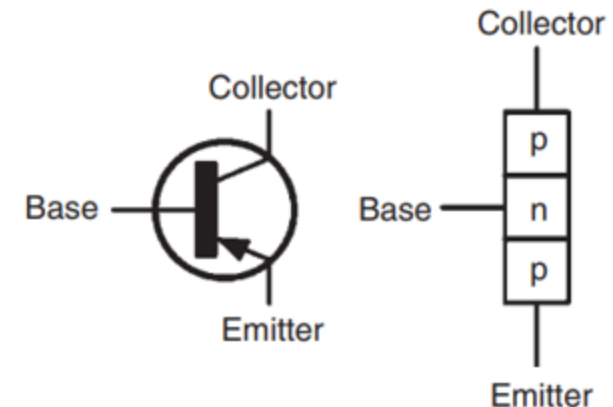

p-n-p transistor



## n-p-n transistor action

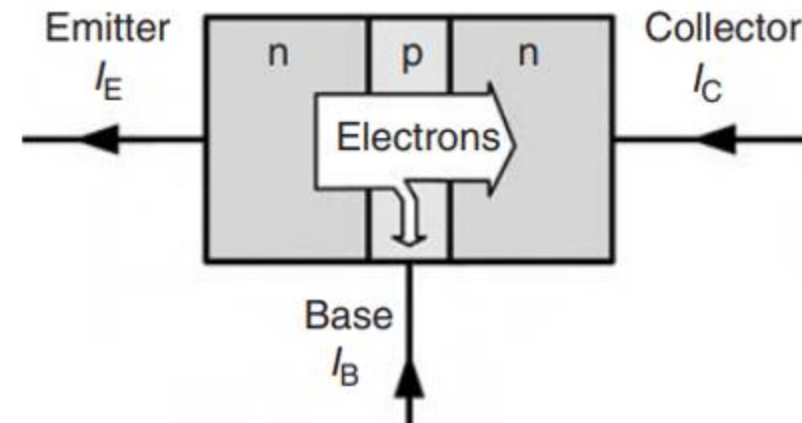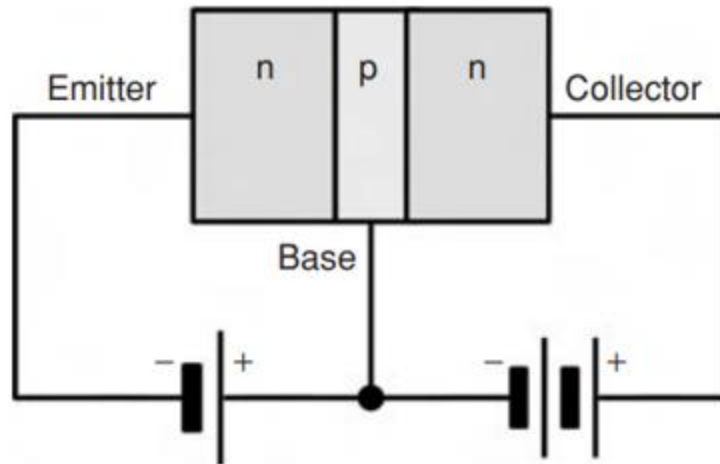- i. Majority carriers in the n-type material are electrons. Base-emitter junction is forward biased, and electrons cross the junction and appear in the base region
- ii. Base region is very thin and lightly doped with holes. Some recombination with holes occurs but many electrons are left in the base region
- iii. These electrons are attracted by the positive potential at the collector terminal
- iv. Most electrons cross into the collector region, creating a collector current.



## p-n-p transistor action

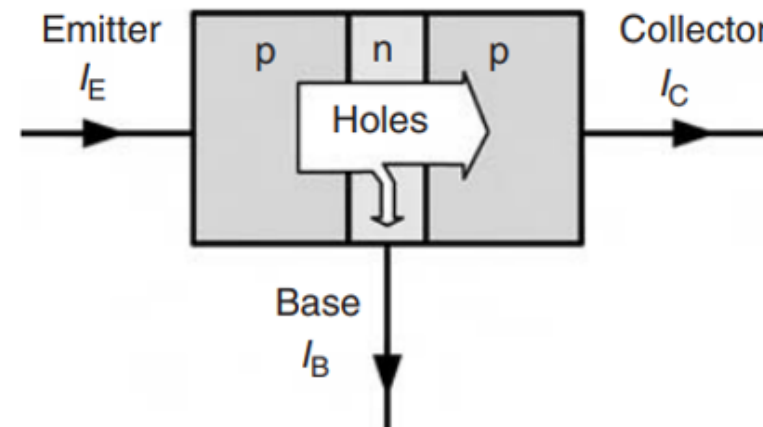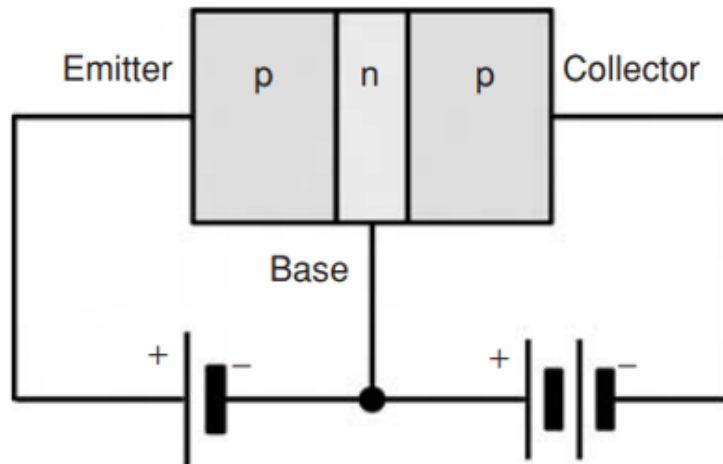- i. Majority carriers in the emitter p-type material are holes. Base-emitter junction is forward biased, and holes cross the junction and appear in the base region
- ii. Base region is very thin and lightly doped with electrons. Although some electron-hole pairs are formed, many holes are left in the base region
- iii. These holes are attracted by the negative potential at the collector terminal
- iv. Majority of the holes cross the base-collector junction, creating a collector current.



# Bias and current flow


- Direction of conventional current flow is from emitter to collector for a p-n-p transistor, and collector to emitter for n-p-n device.

$$I_E = I_B + I_C$$


- A transistor operates with a collector current of 100 mA and an emitter current of 102 mA. Determine base current.

$$I_B = I_E - I_C$$

$$I_B = 102 - 100 = 2mA$$

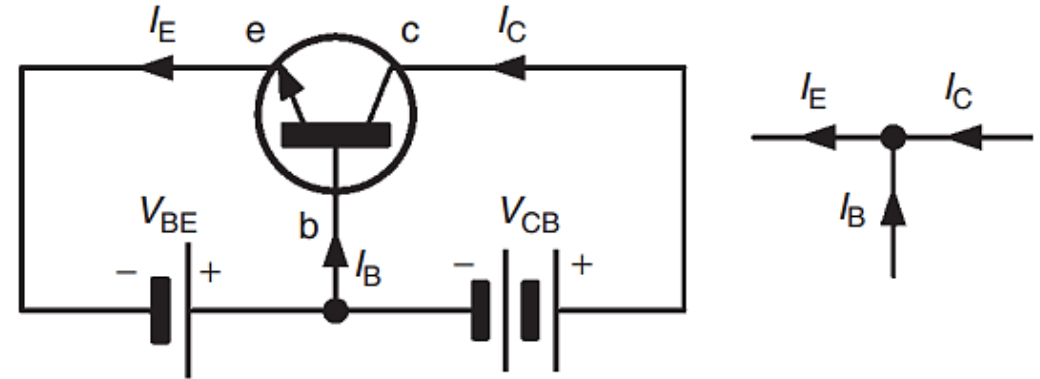

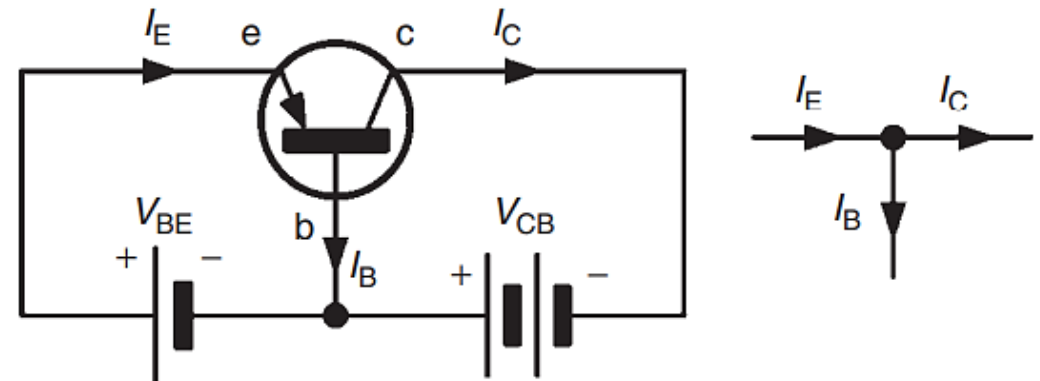
(a) n-p-n bipolar junction transistor (BJT)




(b) p-n-p bipolar junction transistor (BJT)
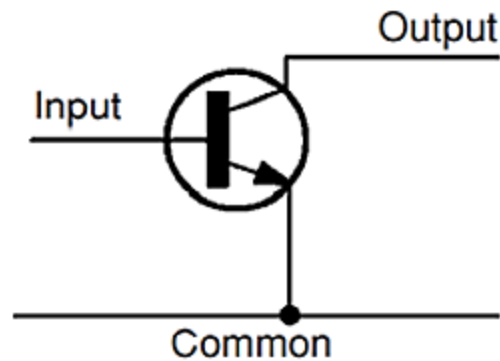
# Transistor operating configurations


- Three basic circuit configurations are used for transistor amplifiers, depending on which transistor connection is common to input and output.
- The configurations are known as common-emitter, common-collector and common-base.
- The n-p-n transistor is more common than the p-n-p transistor and the most popular mode of configuration is the common-emitter mode.



(a) Common emitter

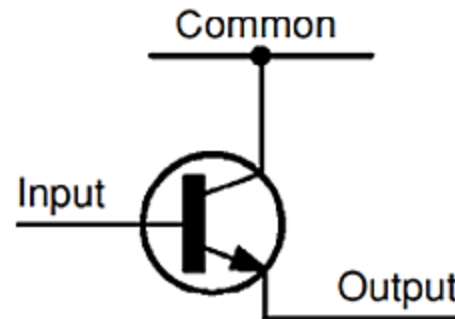

(b) Common collector

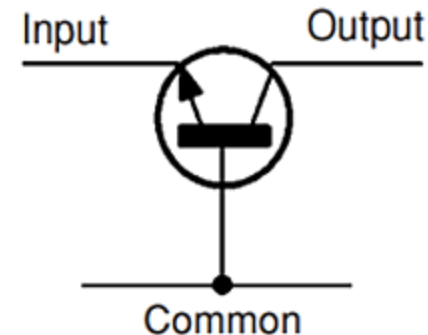

(c) Common base



- In common emitter mode,

$$\beta = \frac{I_C}{I_B}$$

- $\beta$  is the current gain.

$$V_{BE} = V_{BB} - I_B R_B$$


$$V_{CE} = V_{CC} - I_C R_C$$

## Example

- A bipolar junction transistor operates with a base current of 1.2mA and a current gain of 100. Determine the emitter current.

$$I_C = \beta I_B = 100 \times 1.2m = 0.12A$$
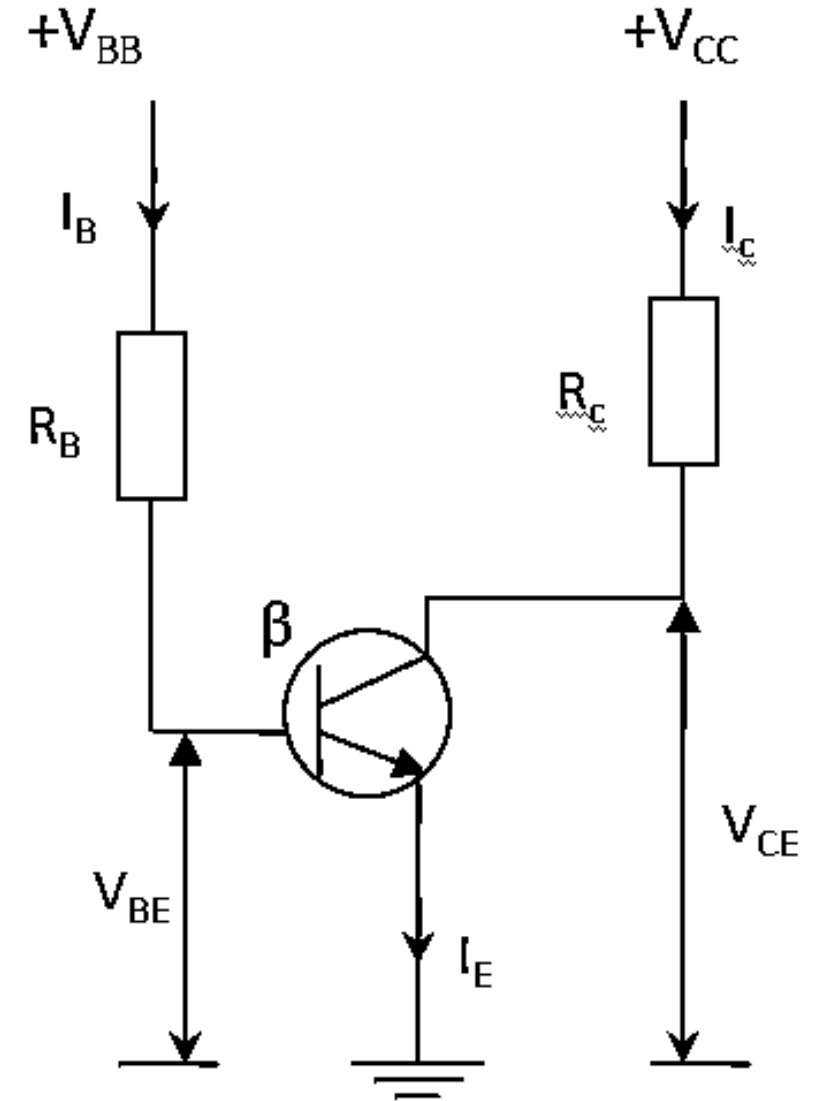
$$I_E = I_B + I_C = 1.2m + 0.12 = 0.1212A$$



## Example

- For the circuit given, neglecting  $V_{BE}$  find:  
 $I_B$ ,  $I_C$ ,  $I_E$  and  $V_{CE}$ .


## Solution

$$I_B = \frac{V_{BB}}{R_B} = \frac{10}{1M} = 10\mu A$$

$$I_C = \beta I_B = 100 \times 10\mu = 1mA$$

$$I_E = I_C + I_B = 10\mu + 1m = 1.01mA$$
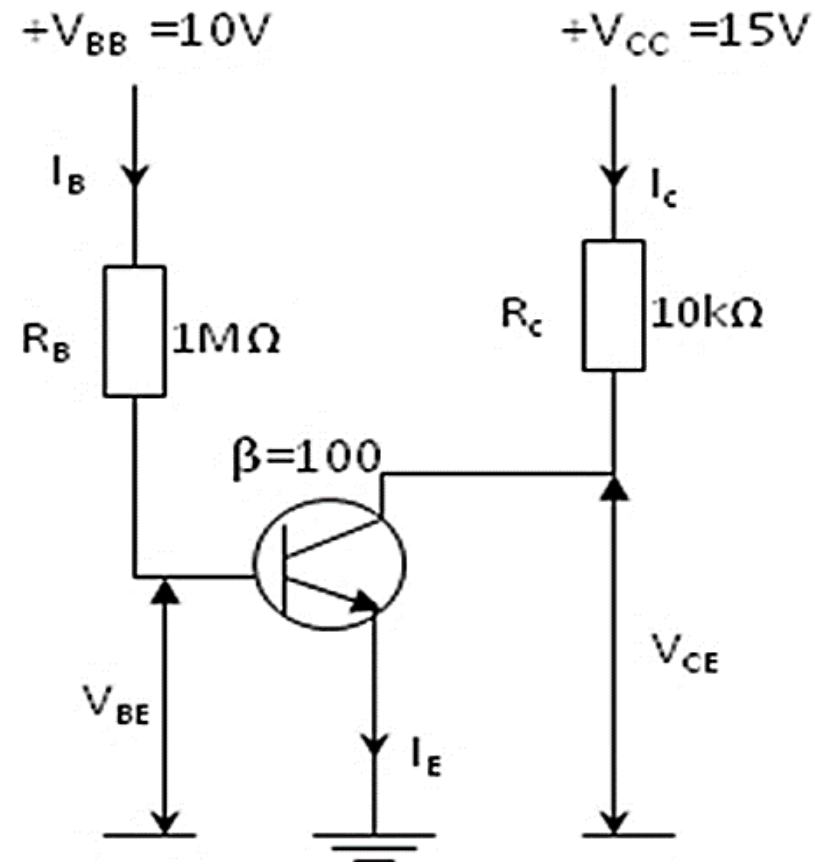
$$V_{CE} = V_{CC} - I_C R_C = 15 - (1m \times 10k) = 5V$$




# Input characteristics

- In CE mode, input current is applied to the base and output current appears in the collector.
- Very little base current flows until the base emitter voltage  $V_{BE}$  exceeds 0.6V.
- Characteristic resembles the forward part of the characteristic for a silicon diode.

i. Static (d.c.) input resistance =  $\frac{V_{BE}}{I_B}$

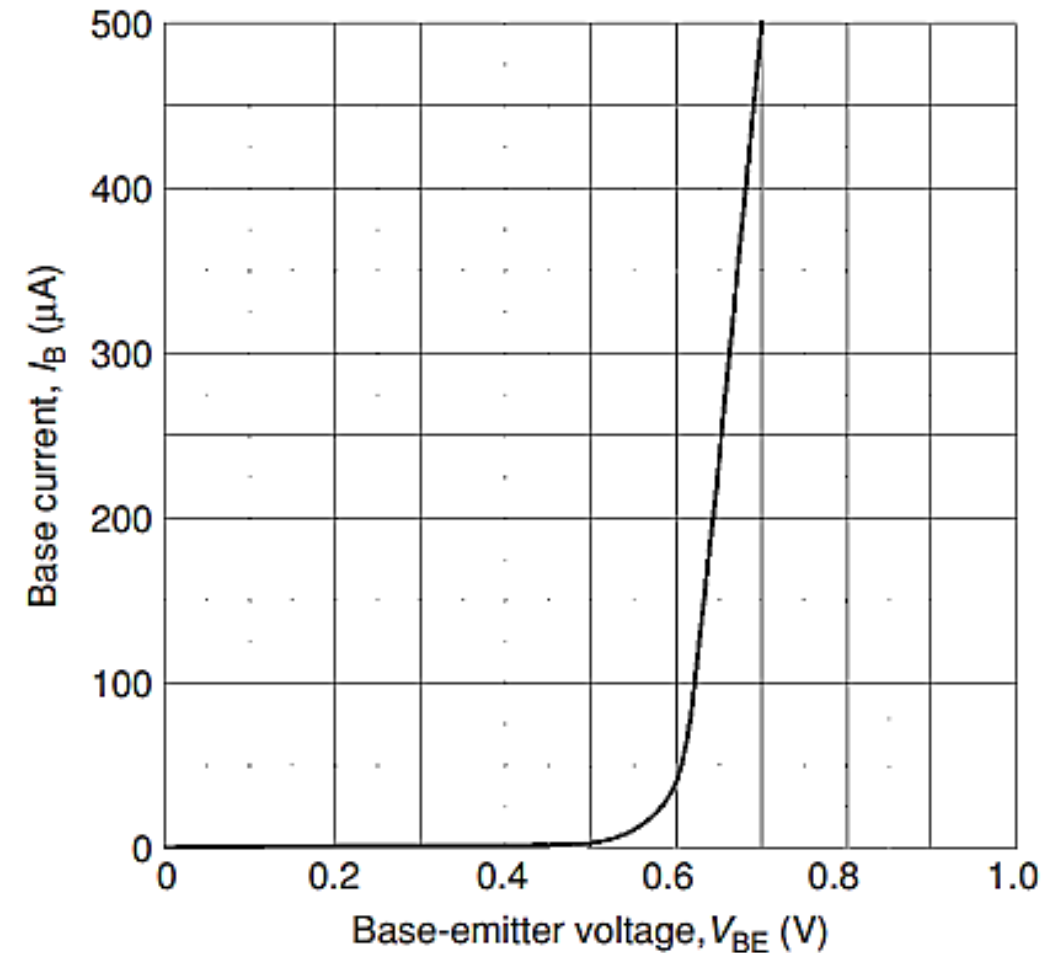ii. Dynamic (a.c.) input resistance =  $\frac{\Delta V_{BE}}{\Delta I_B}$




# Output characteristics

- In output characteristics ( $I_C$  plotted against  $V_{CE}$ ).
- Each curve corresponds to a different value of base current.
- The curves are quite flat; often referred to as constant current characteristic.


- i. Static (d.c.) output resistance =  $\frac{V_{CE}}{I_C}$
- ii. Dynamic (a.c.) output resistance =

$$\frac{\Delta V_{CE}}{\Delta I_C}$$

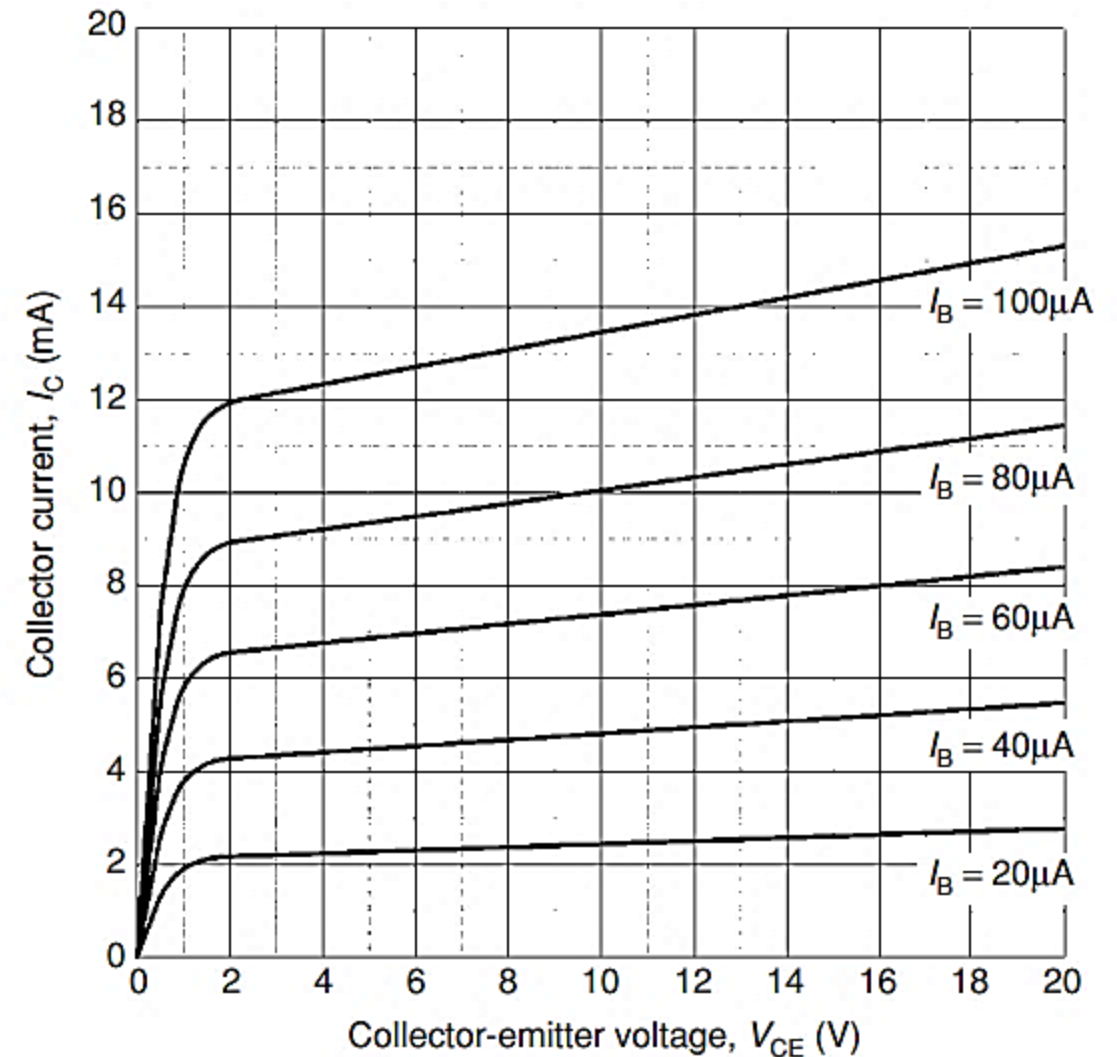
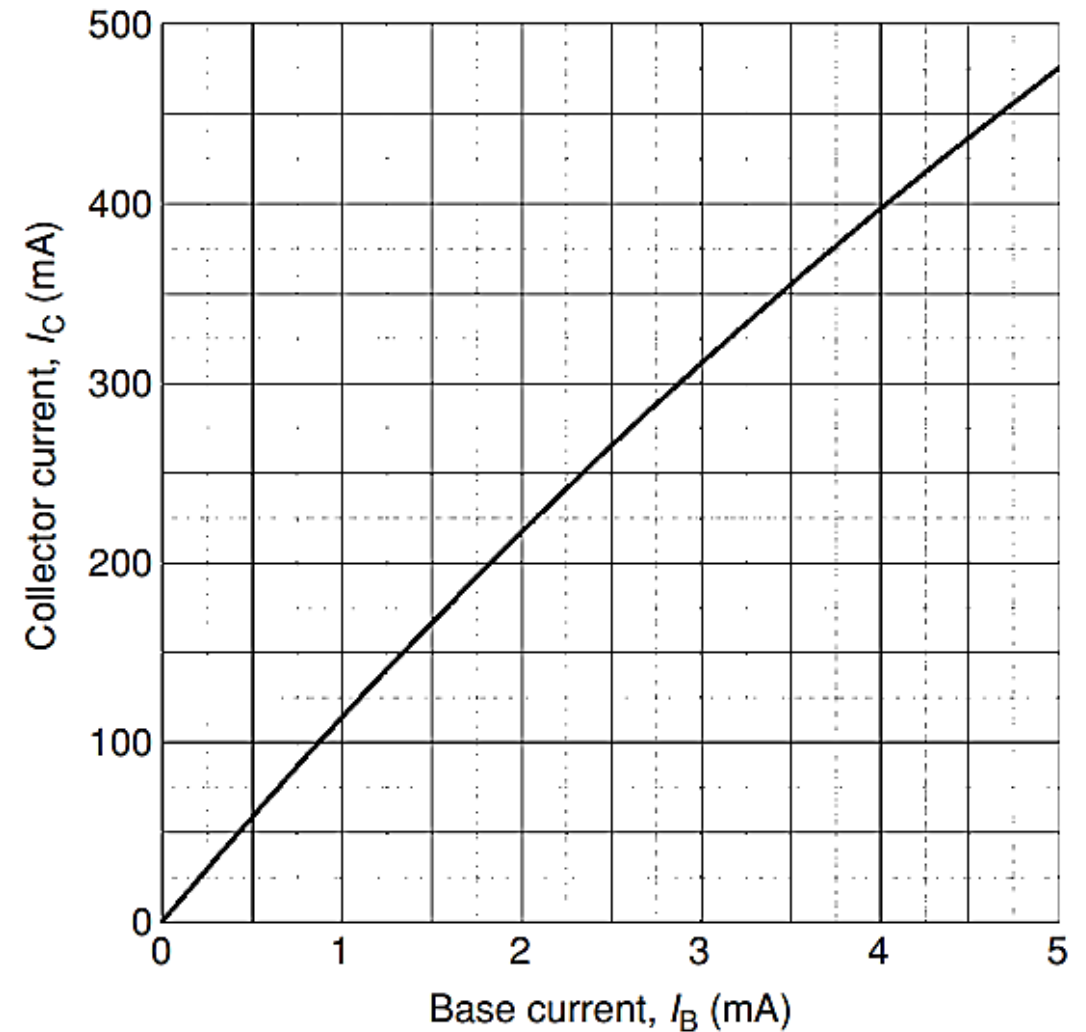
# Transfer characteristics

- A transfer characteristic for an n-p-n bipolar junction transistor plots  $I_C$  against  $I_B$ .
- The slope of this curve (i.e., the ratio of  $I_C$  to  $I_B$ ) is the common-emitter current gain of the transistor.
  - i. Static (or d.c.) current gain =  $\frac{I_C}{I_B}$
  - ii. Dynamic (or a.c.) current gain =  $\frac{\Delta I_C}{\Delta I_B}$



## Example

- When the base-emitter voltage is 0.65V, determine, base current, static and dynamic input resistance.


## Solution

- When  $V_{BE} = 0.65$ ,  $I_B = 250\mu A$ . Static input resistance

$$= \frac{V_{BE}}{I_B} = \frac{0.65}{250\mu} = 2.6k\Omega$$

- $V_{BE}$  changes by 0.06V when  $I_B$  changes by 300 $\mu A$ . Dynamic value of input resistance
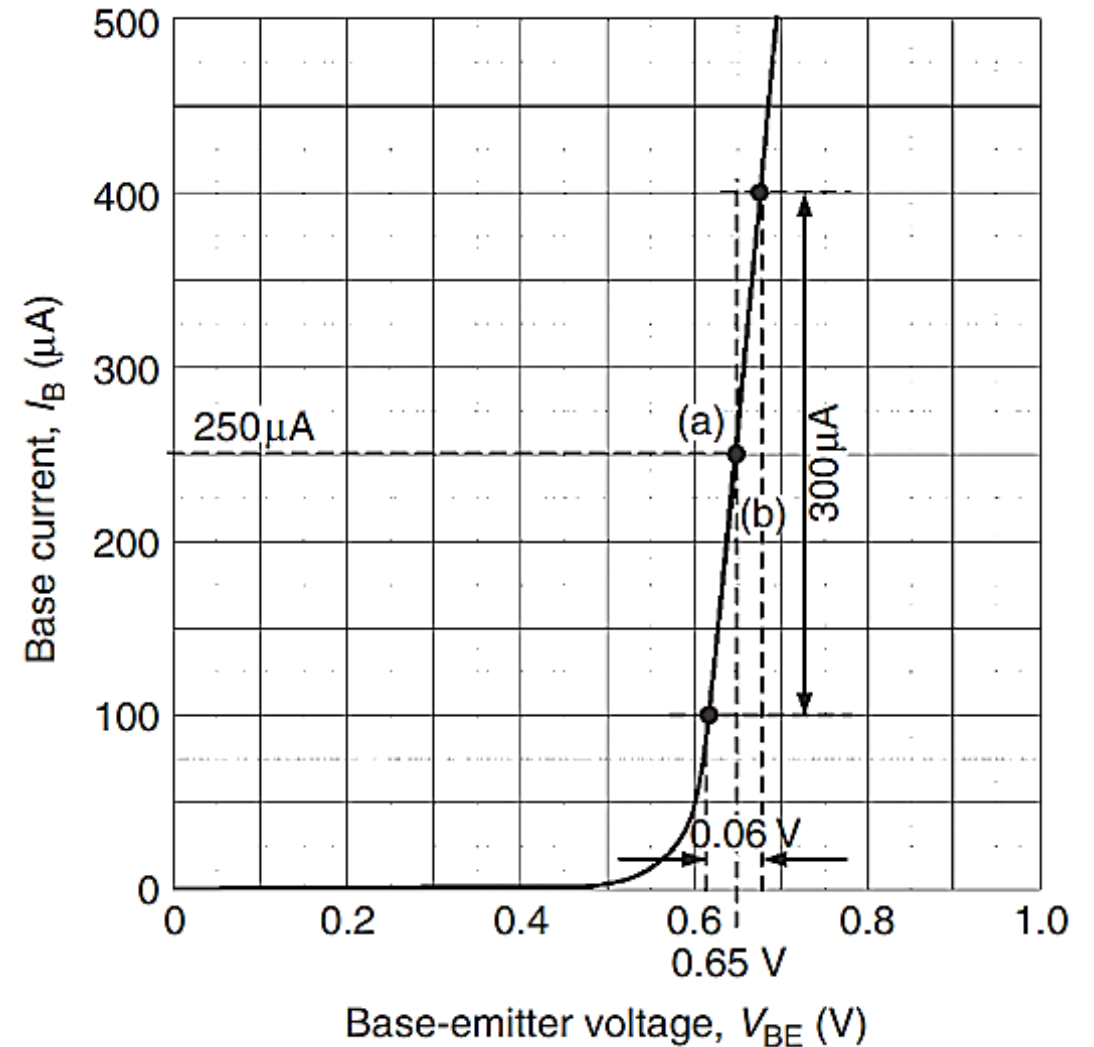
$$= \frac{\Delta V_{BE}}{\Delta I_B} = \frac{0.06}{300\mu} = 200\Omega$$





\*End of session\*



Questions....?