



# BCT 2205 - Lecture 2

✓ Resistors and Capacitors

By J. Mathenge

# Resistance

- Resistance is the **opposition to the flow of current** offered by various components in a circuit.
- The resistance of an electrical conductor is **directly proportional to length, L**, and **inversely proportional to cross-sectional area, A**, i.e.

$$R \propto \frac{L}{A}$$

- Introducing a constant of proportionality,

$$R = \rho \frac{L}{A}$$

- The **constant of proportionality** is known as the resistivity of the material given by the symbol  $\rho$ , in ohmmeter,  $\Omega m$ .

# Examples

- The resistance of 1.5km wire of cross-sectional area  $0.17\text{mm}^2$  is  $150\Omega$ . Determine the resistivity of the wire. (\*ensure you convert all quantities to their S.I. Units)

$$R = \rho \frac{L}{A}; \quad \rho = \frac{RA}{L} = \frac{(150)(0.17\mu)}{1500} = 0.017\mu\Omega\text{m}$$

- Calculate the resistance of 10m length copper wires with a cross-section area of  $1\text{mm}^2$ . Resistivity of copper is  $1.76 \times 10^{-8}\Omega\text{m}$ .


$$R = \rho \frac{L}{A} = \frac{1.76 \times 10^{-8} \times 10}{1 \times 10^{-6}} = 0.176\Omega$$

- Calculate the cross-sectional area of a piece of aluminum wire 100m long and having a resistance of  $2\Omega$ , given resistivity of aluminum is  $0.03 \times 10^{-6}\Omega\text{m}$ .

$$R = \rho \frac{L}{A}; \quad A = \rho \frac{L}{R}; \quad A = \frac{0.03\mu \times 100}{2} = 1.5\text{mm}^2$$

# Resistor Color Coding

- Resistor **color coding represents resistance** using color bands.
- The bands are **nearer to each other on one end** of the resistor than the other; this is the **end we start counting**.

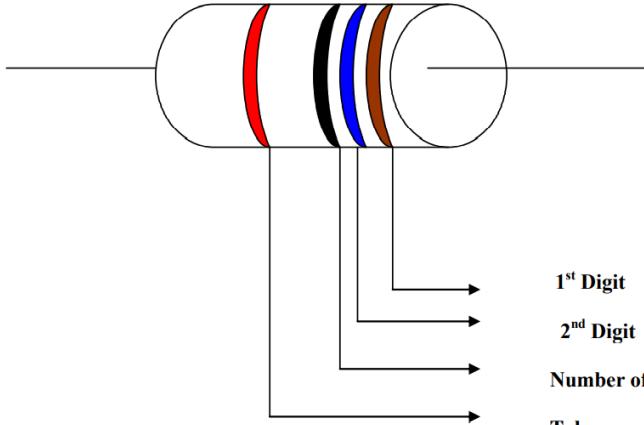Resistor color codes	Color numerical value	Tolerances																				
	<table border="1"><tbody><tr><td>Black - 0</td><td>Green - 5</td></tr><tr><td>Brown - 1</td><td>Blue - 6</td></tr><tr><td>Red - 2</td><td>Violet - 7</td></tr><tr><td>Orange - 3</td><td>Grey - 8</td></tr><tr><td>Yellow - 4</td><td>White - 9</td></tr></tbody></table>	Black - 0	Green - 5	Brown - 1	Blue - 6	Red - 2	Violet - 7	Orange - 3	Grey - 8	Yellow - 4	White - 9	<table border="1"><tbody><tr><td>Brown</td><td><math>\pm 1\%</math></td></tr><tr><td>Red</td><td><math>\pm 2\%</math></td></tr><tr><td>Gold</td><td><math>\pm 5\%</math></td></tr><tr><td>Silver</td><td><math>\pm 10\%</math></td></tr><tr><td>None</td><td><math>\pm 20\%</math></td></tr></tbody></table>	Brown	$\pm 1\%$	Red	$\pm 2\%$	Gold	$\pm 5\%$	Silver	$\pm 10\%$	None	$\pm 20\%$
Black - 0	Green - 5																					
Brown - 1	Blue - 6																					
Red - 2	Violet - 7																					
Orange - 3	Grey - 8																					
Yellow - 4	White - 9																					
Brown	$\pm 1\%$																					
Red	$\pm 2\%$																					
Gold	$\pm 5\%$																					
Silver	$\pm 10\%$																					
None	$\pm 20\%$																					

## Converting from resistance to color bands.

- i.  $36 \times 10^4 \Omega \pm 1\%$  Equals: Orange, Blue, Yellow, Brown
- ii.  $4500\Omega \pm 2\%$  Equals: Yellow, Green, Red, Red.

## Converting from color bands to resistance.

<i>Band</i>	<i>Color</i>	<i>Numeric value</i>
1	Red	2
2	Black	0
3	Orange	$10^3$
4	Brown	$\pm 1\%$
	Equivalent resistance	$20 \times 10^3 \Omega \pm 1\%$

<i>Band</i>	<i>Color</i>	<i>Numeric value</i>
1	Green	5
2	Brown	1
3	Yellow	$10^4$
4	-	$\pm 20\%$
	Equivalent resistance	$51 \times 10^4 \Omega \pm 20\%$

# Resistors in Series

- The source **current** is the same throughout the circuit, i.e.,

$$I = I_{R1} = I_{R2} = I_{R3}$$

- The source **voltage** is equal to the **sum** of all p.d.s across the resistors in the circuit i.e.,


$$V_s = V_{R1} + V_{R2} + V_{R3}$$

$$IR_t = I_{R1}R_1 + I_{R2}R_2 + I_{R3}R_3$$

$$IR_t = I(R_1 + R_2 + R_3)$$

- The total circuit resistance equals the sum of all resistances in the circuit i.e.,

$$R_t = R_1 + R_2 + R_3$$

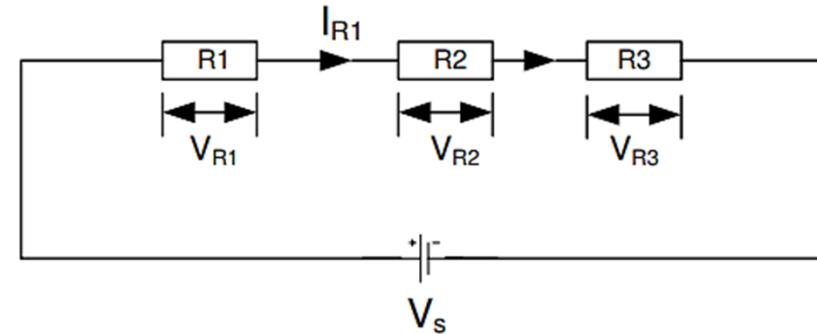

# Example

- Resistors  $R_1 = 900\Omega$ ,  $R_2 = 5K8\Omega$ ,  $R_3 = 7M4\Omega$  are connected in series across voltage supply of 200V.
  - i. Calculate the total resistance.
  - ii. Calculate the total current.
  - iii. Determine the current passing through each of the resistors.
  - iv. Voltage across each resistor.

$$R_t = 900 + 5800 + 7.4M\Omega$$

$$= 7406700\Omega$$

$$I = \frac{V_s}{R_t} = \frac{200}{7406700} = 2.7 \times 10^{-5} A$$

$$V = IR$$

$$V_1 = 2.7 \times 10^{-5} \times 900 = 0.0243 V$$

$$V_2 = 2.7 \times 10^{-5} \times 5.8k = 0.1566 V$$

$$V_3 = 2.7 \times 10^{-5} \times 7.4M = 199.8 V$$

# Resistors in Parallel

- The voltage in a parallel circuit remains the same across any branch i.e.,

$$V_s = V_{R1} = V_{R2} = V_{R3}$$

- The total circuit current is the sum of all the branch currents i.e.,


$$I_t = I_{R1} + I_{R2} + I_{R3}$$

$$I_t = \frac{V_{R1}}{R_1} + \frac{V_{R2}}{R_2} + \frac{V_{R3}}{R_3}$$

$$I_t = V_s \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

- The circuit resistance is obtained using
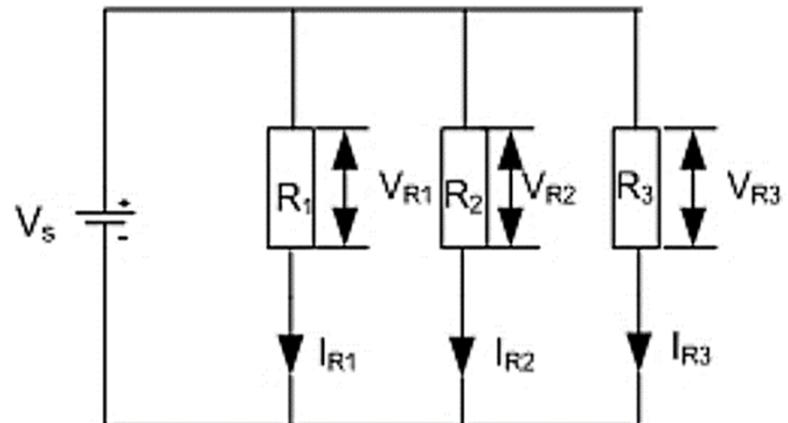
$$\frac{1}{R_t} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$



# Example

- Resistors  $R_1 = 900\Omega$ ,  $R_2 = 5K8\Omega$ ,  $R_3 = 7M4\Omega$  are connected in parallel across voltage supply of 200V.
  - Calculate the total resistance.
  - Calculate the total current.
  - Determine the current passing through each of the resistors.
  - Current through each resistor.

$$\frac{1}{R_t} = \left( \frac{1}{900} + \frac{1}{5800} + \frac{1}{7.4M} \right)$$

$$R_t = 779.022\Omega$$

$$I_t = \frac{V_s}{R_t} = \frac{200}{779.022} = 0.257 A$$

$$V_{Rt} = V_{R1} = V_{R2} = V_{R3} = 200V$$

$$I_{R1} = \frac{V_{R1}}{R_1} = \frac{200}{900} = 0.222 A$$

$$I_{R2} = \frac{V_{R2}}{R_2} = \frac{200}{5800} = 0.034 A$$


$$I_{R3} = \frac{V_{R3}}{R_3} = \frac{200}{7.4M} = 2.703 \times 10^{-5} A$$

# Capacitors

- A capacitor consists of two plates separated by an insulating material known as a dielectric.
- Capacitors are simple passive devices used to store electric charge on their plates when connected to a voltage source.
- Capacitors can be used in different applications and circuits mostly to maintain the voltage at a certain level.



A Typical Capacitor

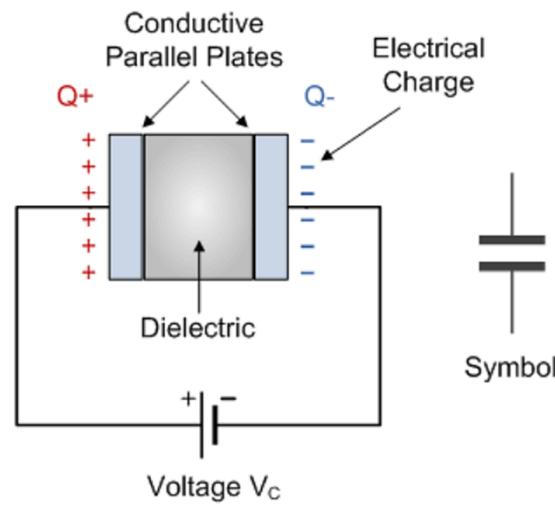


# Capacitance

- The plates of capacitor are connected to a battery of V volts, where d is the distance between the plates.
- The property of a capacitor to store charge is called capacitance, C.

$$C = \frac{Q}{V}$$

- The unit of capacitance is the farad F.
- The charge Q stored in a capacitor is given by,

$$Q = I \times t \text{ Coulombs}$$

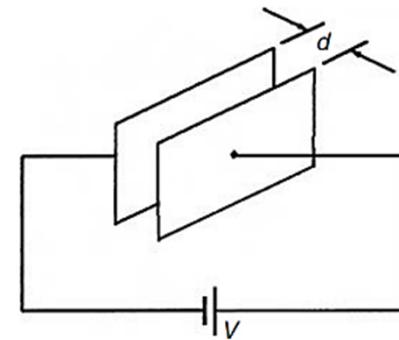

## Examples

- Determine the p.d. across a 4  $\mu\text{F}$  capacitor when charged with 5 mC.

$$V = \frac{Q}{C} = \frac{5m}{4\mu} = 1.25\text{kV}$$

- Find the charge on a 50pF capacitor when the voltage applied to it is 2 kV.

$$Q = CV = 50 \times 10^{-12} \times 2k = 100 \times 10^{-9}C = 0.1\mu C$$

- A direct current of 4A flows into a previously uncharged 20 $\mu\text{F}$  capacitor for 3ms. Determine the p.d. between the plates.

$$Q = It = 4 \times 3m = 12mC$$

$$Q = CV; \quad V = \frac{Q}{C} = \frac{12m}{20\mu} = 600V$$

# Capacitors in parallel

- The applied voltage is common to all capacitors i.e.,

$$V_s = V_{c1} = V_{c2} = V_{c3}$$


- However, the current through each capacitor is different, thus, the charge developed across each capacitor is different.
- The total charge is the sum of charges in each capacitor, i.e.,

$$Q_t = Q_{c1} + Q_{c2} + Q_{c3}$$

- Using  $Q = CV$

$$V_s C_t = V_s (C_1 + C_2 + C_3)$$

$$C_t = C_1 + C_2 + C_3$$

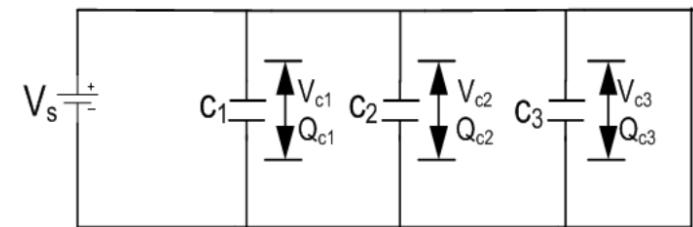

# Example

- Capacitances  $1\mu F$ ,  $3\mu F$ ,  $5\mu F$  and  $6\mu F$  are connected in parallel to a voltage supply of 100V. Determine the:
  - i. Equivalent circuit capacitance
  - ii. Total charge
  - iii. Charge on each capacitor

$$C = 1 + 3 + 5 + 6 = 15\mu F$$

$$Q = CV = 15\mu \times 100 = 1.5mC$$

$$Q_1 = C_1 V = 1\mu \times 100 = 0.1mC$$

$$Q_2 = C_2 V = 3\mu \times 100 = 0.3mC$$

$$Q_3 = C_3 V = 5\mu \times 100 = 0.5mC$$

$$Q_4 = C_4 V = 6\mu \times 100 = 0.6mC$$

# Capacitors in series

- In a series circuit, charge  $Q$  is constant since current flowing is the same through the capacitors, i.e.,

$$Q_t = Q_{c1} = Q_{c2} = Q_{c3}$$

- However, voltage across the capacitors is different. The applied voltage,

$$V_s = V_{c1} + V_{c2} + V_{c3}$$

- From  $V = Q/C$

$$V_s = \frac{Q_t}{C_t} = \frac{Q_{c1}}{C_1} + \frac{Q_{c2}}{C_2} + \frac{Q_{c3}}{C_3}$$

$$\frac{1}{C_t} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

# Example

- i. Capacitances of  $3\mu F$ ,  $6\mu F$  and  $12\mu F$  are connected in series across a 350V supply. Calculate:
  - a. The equivalent capacitance
  - b. Charge on each capacitor
  - c. Voltage across each capacitor

$$\frac{1}{C} = \frac{1}{3} + \frac{1}{6} + \frac{1}{12} = \frac{7}{12} \quad ; C = \frac{12}{7} \mu F$$

$$Q = CV = \frac{12}{7} \mu \times 350 = 0.6mC$$

- Voltage across each capacitor

$$V_1 = \frac{Q}{C_1} = \frac{0.6m}{3\mu} = 200V$$

$$V_2 = \frac{Q}{C_2} = \frac{0.6m}{6\mu} = 100V$$

$$V_3 = \frac{Q}{C_3} = \frac{0.6m}{12\mu} = 50V$$



\*End of session\*



Questions....?