



BCT 2205 - Lecture 6


✓ **DC Transients**

By J. Mathenge

Introduction

- When a DC voltage is applied to a capacitor C and resistor R connected in series, there is a short period of time immediately after the voltage is connected, during which the current and voltage across C and R are changing.
- Similarly, when a DC voltage is connected to a circuit having inductance L connected in series with resistance R , there is a short period of time immediately after the voltage is connected, during which the current and the voltage across L and R are changing.
- These changing values are called **transients**.

C-R circuit

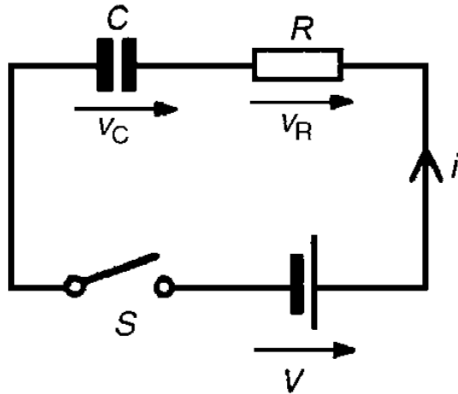

- When switch S is closed, by Kirchhoff's voltage law,

$$V = v_C + v_R \quad (1)$$

- Written as,

$$V = \frac{q}{C} + iR \quad (2)$$

- At the instant of closing S , assuming there is no initial charge on the capacitor, q_0 is zero, hence v_{C0} is zero.

$$V = 0 + v_{R0}$$

$$V = v_{R0}$$

- The initial current flowing,


$$i_0 = I = \frac{V}{R}$$

- A short time later at time t_1 after closing S , the capacitor is partly charged to q_1 because current has been flowing.


$$V = \frac{q_1}{C} + i_1 R$$

- A short time later, say t_2 after closing the switch, the charge has increased to q_2 and v_C has increased to $(\frac{q_2}{C})$ volts.
- Since $V = v_C + v_R$ and V is a constant, as v_C increase, v_R decreases.
- A few seconds after closing S , the capacitor is fully charged and current no longer flows,

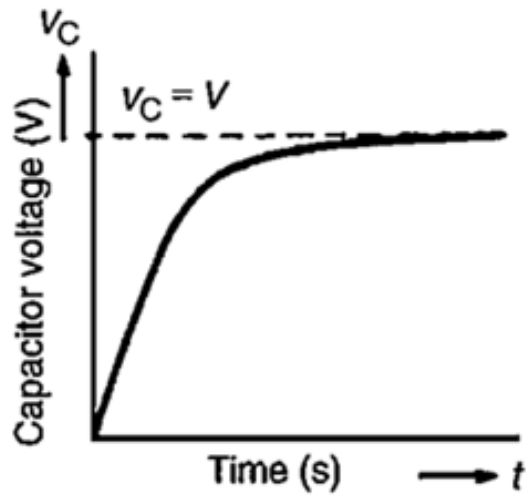
$$i = 0, \quad v_R = iR = 0, \quad v_C = V$$



(a) Capacitor voltage transient

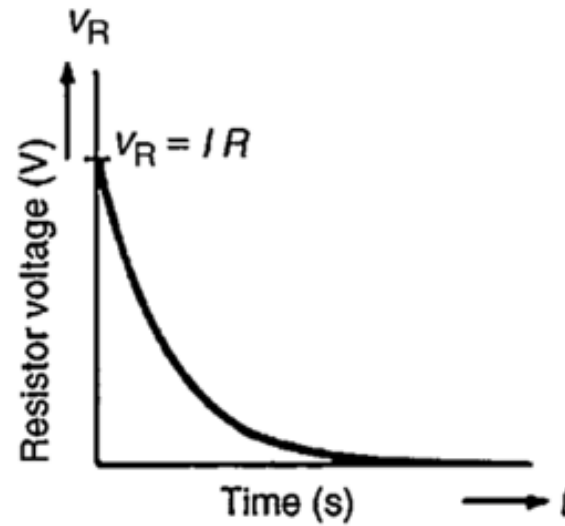


(b) Resistor voltage transient

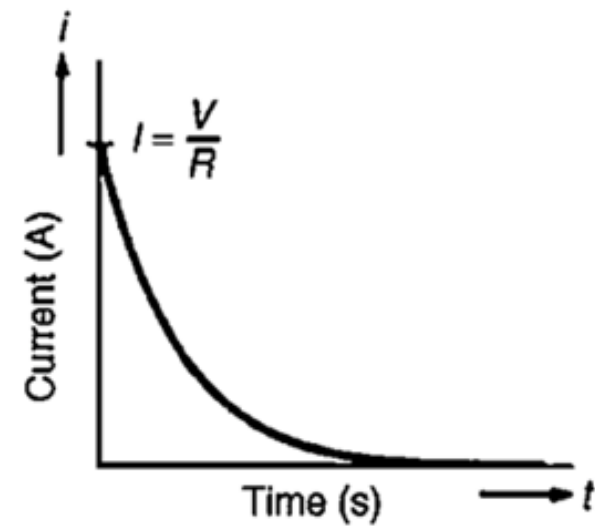

(c) Current transient

Time constant for a $C - R$ circuit

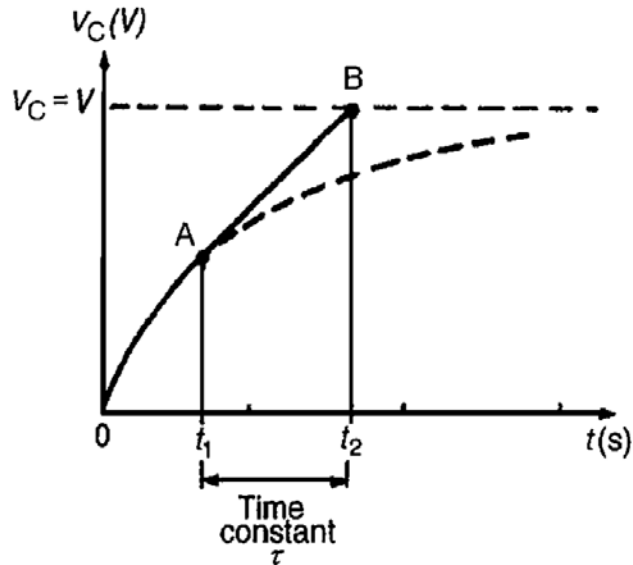

- Let voltage be varied such that **current** flowing in the circuit is **constant**.
- The curve will follow tangent AB.
- Let the capacitor voltage reach its final value at t_2 seconds.

- $(t_2 - t_1)$ is called the **time constant** of the circuit, denoted by τ .

$$\tau = CR \text{ seconds}$$

1. Growth of capacitor voltage

$$v_C = V(1 - e^{-\frac{t}{CR}}) = V(1 - e^{-t/\tau})$$

2. Decay of resistor voltage

$$v_R = Ve^{-\frac{t}{CR}} = Ve^{-t/\tau}$$

3. Decay of resistor current

$$i = Ie^{-\frac{t}{CR}} = Ie^{-t/\tau}$$

Example

- A circuit consists of a resistor connected in series with a $0.5\mu\text{F}$ capacitor and has a time constant of 12ms . Determine:
 - i. the value of the resistor,
 - ii. the capacitor voltage, 7 ms after connecting the circuit to a 10 V supply.
- The time constant

$$\tau = CR \quad ; \quad R = \frac{\tau}{C} = \frac{12\text{m}}{0.5\mu} = 24\text{k}\Omega$$

- The equation for growth of capacitor voltage

$$\begin{aligned} v_c &= V\left(1 - e^{-\frac{t}{\tau}}\right) \quad ; \quad \tau = 12\text{ms} \quad ; \quad v_c = 10\left(1 - e^{-\frac{7\text{m}}{12\text{m}}}\right) \\ &= 10(1 - e^{-0.583}) = 10(1 - 0.558) = 4.42\text{V} \end{aligned}$$

- A 20 μF capacitor is connected in series with a 50 $\text{k}\Omega$ resistor and the circuit is connected to a 20 V, DC supply. Determine:

1. The initial value of the current flowing

$$I = \frac{V}{R} = \frac{20}{50K} = 0.4\text{mA}$$

2. Time constant of the circuit

$$\tau = CR = (20\mu)(50k) = 1\text{s}$$

3. Value of current one second after connection

$$i = Ie^{-t/\tau} = 0.4e^{-1/1} = 0.4 \times 0.368 = 0.147\text{mA}$$

4. Capacitor voltage two seconds after connection

$$\begin{aligned} v_c &= V(1 - e^{-\frac{t}{\tau}}) = 20(1 - e^{-\frac{2}{1}}) \\ &= 20(1 - 0.135) = 18.3\text{V} \end{aligned}$$

5. The time after connection when resistor voltage is 15 V

$$v_R = Ve^{-t/\tau}; 15 = 20e^{-t/1}$$


$$\frac{3}{4} = e^{-t} ; \frac{4}{3} = e^t$$

- Taking natural logarithms of each side

$$\ln \frac{4}{3} = t \ln e ; t = \ln \frac{4}{3} ; t = 0.288\text{ s}$$

Discharging a capacitor

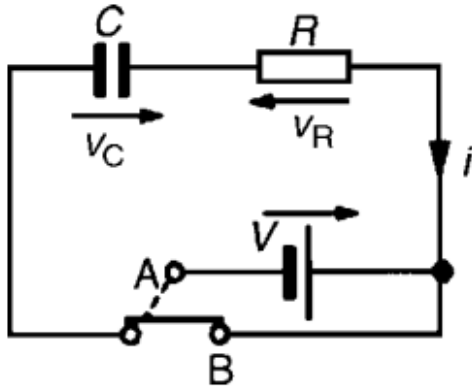- When a capacitor is charged and the switch is then moved to position B, the electrons stored in the capacitor keep the current flowing for a short time.



- Initially, $v_C = v_R = V$, and $i = I = V/R$.
- During the transient decay, $v_C = v_R$.


- Finally, the transients decay exponentially to zero, $v_C = v_R = 0$.

- Decay of voltage,


$$v_C = Ve^{(-t/CR)} = Ve^{(-t/\tau)}$$

- Decay of current,

$$i = Ie^{(-t/CR)} = Ie^{(-t/\tau)}$$

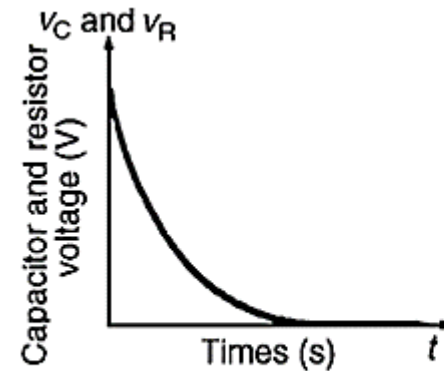


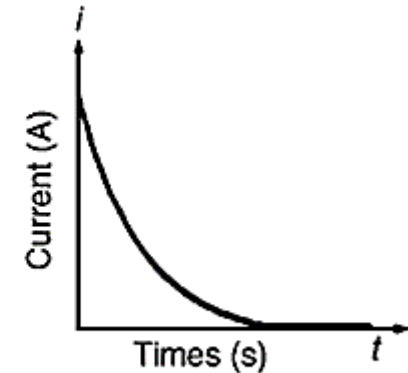(a) Capacitor and resistor voltage transient



(b) Current transient

Current growth in L – R circuit

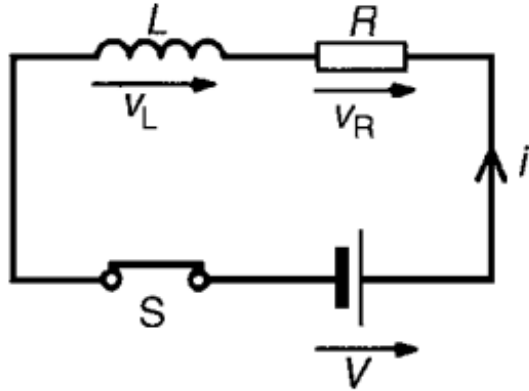

$$V = v_L + v_R \quad (1)$$

$$V = L \frac{di}{dt} + iR \quad (2)$$


- At the instant of closing the switch,
 $V = v_L + 0$; $V = v_L$
- At t_1 after closing S,

$$V = L \frac{di_1}{dt_1} + i_1 R$$


- At t_2 seconds after closing the switch, the current flowing is i_2 .

- Since v_R increases, v_L decreases.
- At steady state, current flow is entirely limited by R.

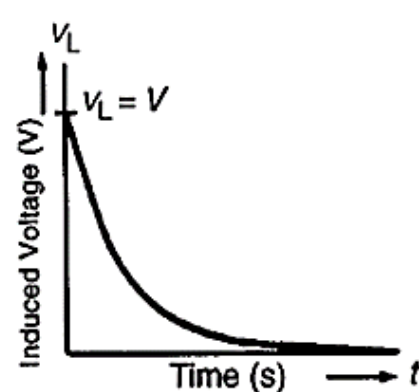
$$I = \frac{V}{R}, \quad v_R = IR; \quad v_L = 0$$



(a) Induced voltage transient

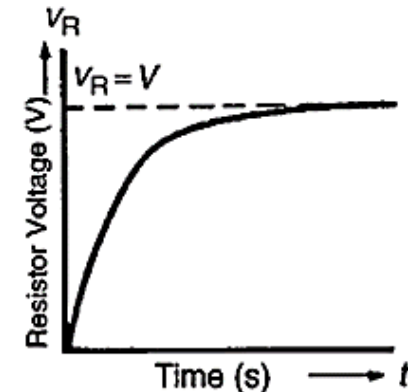

(b) Resistor voltage transient

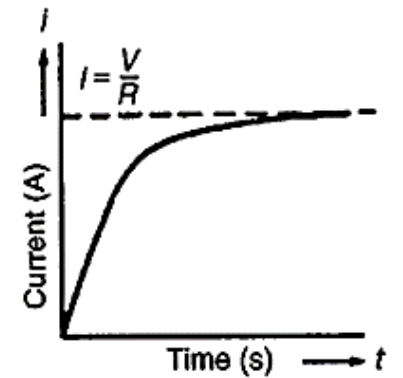

(c) Current transient

Time constant for an L – R circuit

- The time constant of a series connected L – R circuit is given by:

$$\text{time constant } \tau = \frac{L}{R} \text{ seconds}$$

1. Decay of induced voltage

$$v_L = V e^{(-Rt/L)} = V e^{(-t/\tau)}$$


2. Growth of resistor voltage

$$v_R = V(1 - e^{(-\frac{Rt}{L})}) = V(1 - e^{(-\frac{t}{\tau})})$$

3. Growth of current flow

$$i = I(1 - e^{(-\frac{Rt}{L})}) = I(1 - e^{(-\frac{t}{\tau})})$$

Current decay in an L – R circuit

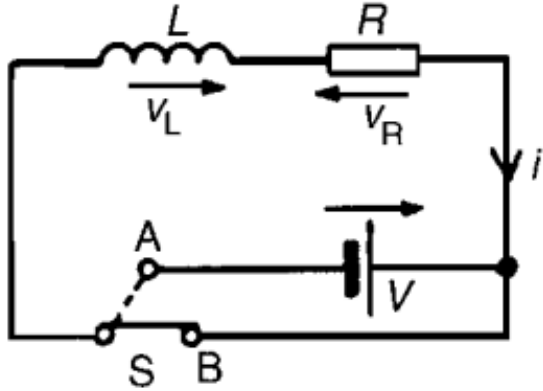

- When S is moved to position B , the current value decreases, causing a decrease in the strength of the magnetic field.
- Flux linkages occur, generating a voltage

$$v_L = L(di/dt)$$

- This voltage keeps current i flowing in the circuit, its value limited by R .

$$v_L = v_R$$

- The current decays exponentially to zero.
- v_L also decays exponentially to zero.
- Decay of voltages,

$$v_L = v_R = Ve^{(-Rt/L)} = Ve^{(-t/\tau)}$$

- Decay of current,

$$i = Ie^{(-Rt/L)} = Ie^{(-t/\tau)}$$

Example

- Find the current in a series RL circuit having $R = 2\Omega$ and $L = 10H$ when a DC voltage of 100V is applied.

$$\tau = 10/2 = 5 \text{ s}$$

- The current in a series LR circuit after the sudden application of a DC voltage is,

$$i(t) = \frac{V}{R} \left(1 - e^{-\frac{t}{\tau}} \right)$$

- Find the value of the current 5s after the application of the DC voltage.

$$i(t) = \frac{100}{2} \left(1 - e^{-\frac{5}{5}} \right) = 50 (1 - e^{-1}) = 50 \left(1 - \frac{1}{e} \right) = 31.48A$$

- An inductor has an inductance of 200 mH and is connected in series with a 1 kΩ resistor to a 24V, DC supply. Determine,

1. time constant of the circuit

$$\tau = \frac{L}{R} = \frac{0.2}{1000} = 0.2 \text{ ms}$$

2. steady-state value of the current flowing

$$I = \frac{V}{R} = \frac{24}{1000} = 24 \text{ mA}$$

3. current flowing in the circuit at a time equal to one time constant,

$$i = I(1 - e^{-\frac{t}{\tau}}) ; t = 1\tau$$

$$\begin{aligned} i &= 24(1 - e^{-\frac{1\tau}{\tau}}) \\ &= 24(1 - e^{-1}) = 15.17 \text{ mA} \end{aligned}$$

4. voltage drop across the inductor at a time equal to two-time constants

$$\begin{aligned} t &= 2\tau, \quad v_L = 24e^{-2\tau/\tau} \\ &= 24e^{-2} = 3.248 \text{ V} \end{aligned}$$

5. voltage drop across the resistor after a time equal to three-time constants.

$$\begin{aligned} v_R &= V(1 - e^{-\frac{t}{\tau}}) ; \text{ when } t = 3\tau, \\ v_R &= 24(1 - e^{-\frac{3\tau}{\tau}}) = 22.81 \text{ V} \end{aligned}$$



End of session



Questions....?