



BCT 2205 - Lecture 5


✓ DC circuit theory - II

By J. Mathenge

Thévenin's theorem


- *The current in any branch of a network is that which would result if an e.m.f. equal to the p.d. across a break made in the branch, were introduced into the branch, all other e.m.f.'s being removed and represented by the internal resistances of the sources.*
 - i. remove the resistance R from that branch,
 - ii. determine the open-circuit voltage, E , across the break,
 - iii. remove each source of e.m.f. and replace them by their internal resistances and then determine the resistance, r , 'looking-in' at the break,
 - iv. determine the value of the current from the equivalent circuit shown, i.e.,

$$I = \frac{E}{R+r}$$

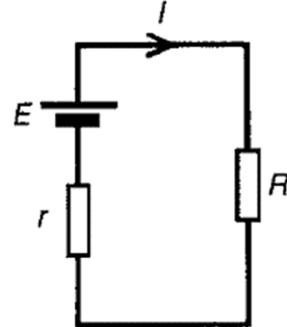


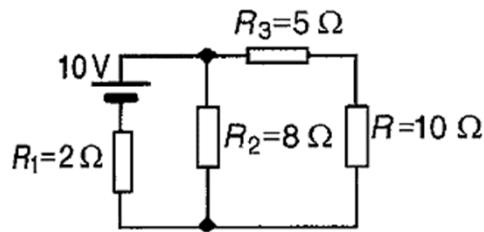Example

- Use Thévenin's theorem to find current flowing in the $10\ \Omega$ resistor for the circuit




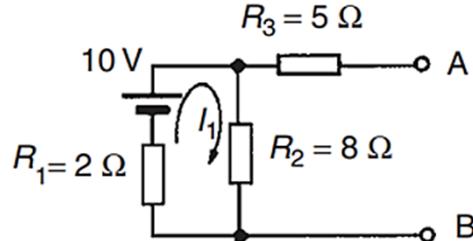- The $10\ \Omega$ resistance is removed from the circuit



$$I_1 = \frac{10}{R_1 + R_2} = \frac{10}{2 + 8} = 1\text{ A}$$

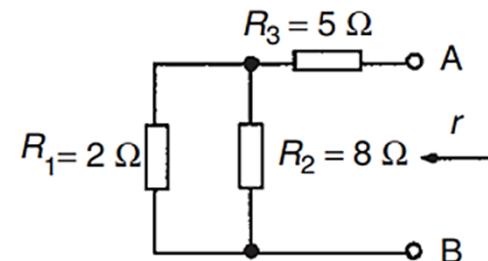- P.d. across $R_2 = I_1 R_2 = 1 \times 8 = 8\text{ V}$.
- Hence p.d. across AB, i.e., the open-circuit voltage across the break, $E = 8\text{ V}$
- Removing the source of e.m.f. gives the circuit



- Resistance,



$$r = R_3 + \frac{R_1 R_2}{R_1 + R_2}$$

$$= 5 + \frac{2 \times 8}{2 + 8} = 5 + 1.6 = 6.6\Omega$$

- The equivalent Thévenin's circuit is shown


$$I = \frac{E}{R + r} = \frac{8}{10 + 6.6}$$

$$= \frac{8}{16.6} = 0.482 \text{ A}$$

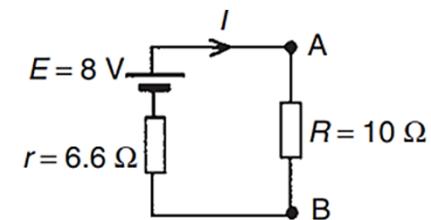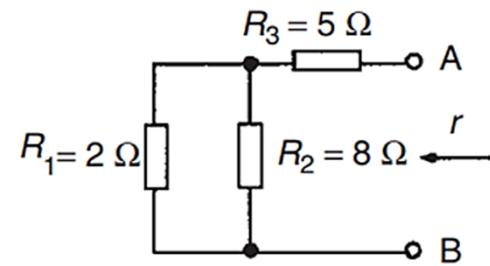


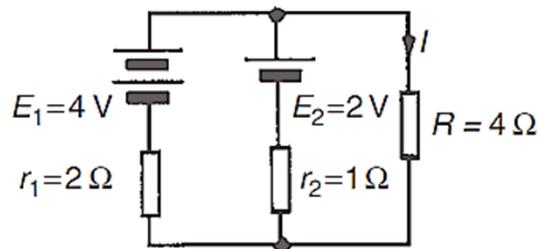Example

- Use Thévenin's theorem to determine the current flowing in the 4Ω resistor. Find also the power dissipated in the 4Ω resistor.



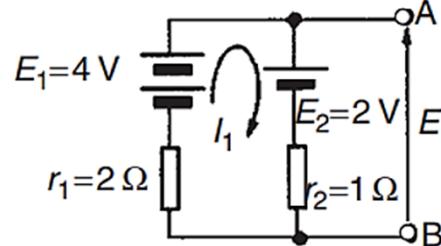- The 4Ω resistor is removed from the circuit




- Current

$$I_1 = \frac{E_1 - E_2}{r_1 + r_2} = \frac{4 - 2}{2 + 1} = \frac{2}{3} \text{ A}$$

- P.d across AB,

$$E = E_2 + I_1 r_2 = 2 + \frac{2}{3}(1) = 2\left(\frac{2}{3}\right) \text{ V}$$

- Removing the sources of e.m.f. gives

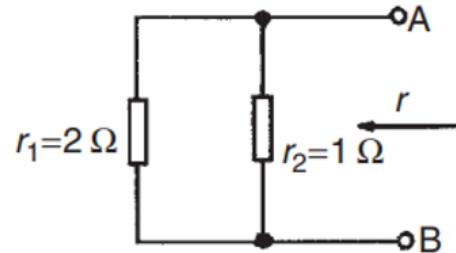

- Resistance



$$r = \frac{2 \times 1}{2 + 1} = \frac{2}{3} \Omega$$

- Current in the 4Ω resistor

$$\begin{aligned} I &= \frac{E}{r + R} = \frac{2 \left(\frac{2}{3} \right)}{\frac{2}{3} + 4} \\ &= \frac{8/3}{14/3} = \frac{8}{14} = 0.571 \text{ A} \end{aligned}$$


- Power dissipated in the 4Ω resistor,
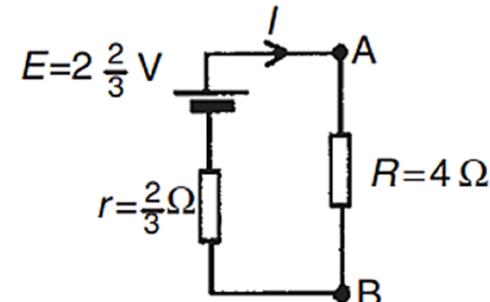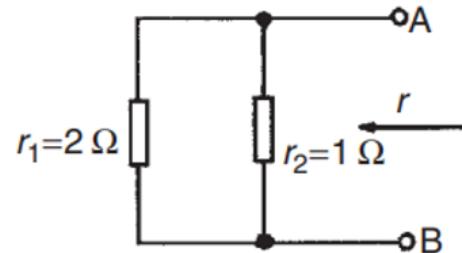
$$P = I^2 R = (0.571^2)4 = 1.304 \text{ W}$$



Constant-current source


- Thévenin constant-voltage source consisted of a constant e.m.f. in series with an internal resistance.
- A source of electrical energy can also be represented by a constant-current source in parallel with a resistance.
 - i. An ideal constant-voltage generator is one with zero internal resistance so that it supplies the same voltage to all loads.
 - ii. An ideal constant-current generator is one with infinite internal resistance so that it supplies the same current to all loads.

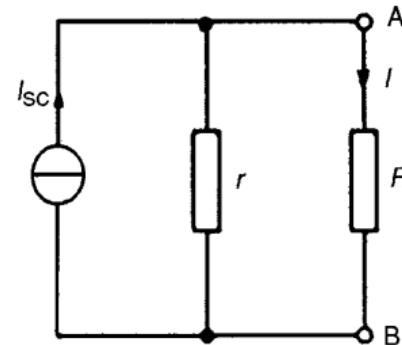

Norton's theorem


- *The current that flows in any branch of a network is the same as that which would flow in the branch if it were connected across a source of electrical energy, the short-circuit current of which is equal to the current that would flow in a short-circuit across the branch, and the internal resistance of which is equal to the resistance which appears across the open-circuited branch terminals.*
 - i. short-circuit branch AB,
 - ii. determine the short-circuit current I_{SC} flowing in the branch,
 - iii. remove all sources of e.m.f. and replace them by their internal resistance, then determine the resistance r , 'looking-in' at a break made between A and B
 - iv. determine the current flowing in resistance R from the Norton equivalent network.
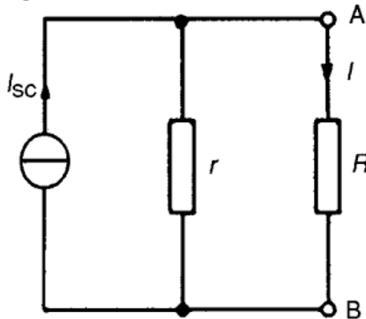
$$I = \left(\frac{r}{r+R} \right) I_{SC}$$





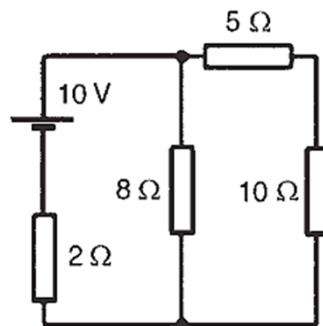Example

- Use Norton's theorem to determine the current flowing in the $10\ \Omega$ resistance for the circuit



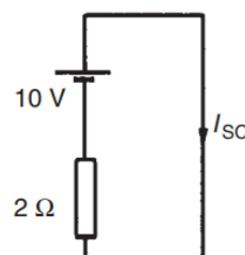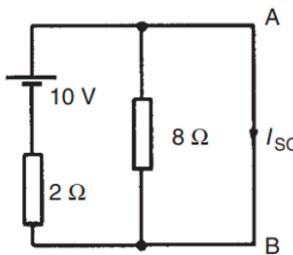
- The branch containing the $10\ \Omega$ resistance is short-circuited



$$I_{SC} = \frac{10}{2} = 5\ A$$

- If the $10\ V$ source of e.m.f. is removed, the resistance 'looking-in' is given by
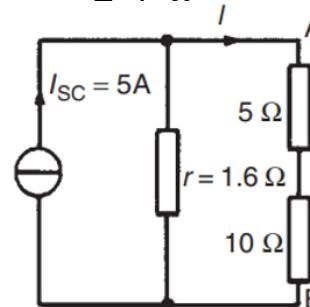
$$r = \frac{2 \times 8}{2 + 8} = 1.6\ \Omega$$




- Current in the $10\ \Omega$ resistance,


$$I = \left(\frac{1.6}{1.6 + 5 + 10} \right) (5) = 0.482\ A$$

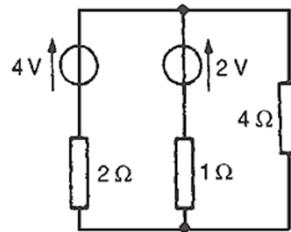Example

- Use Norton's theorem to determine current flowing in the 4Ω resistance



- The 4Ω branch is short-circuited

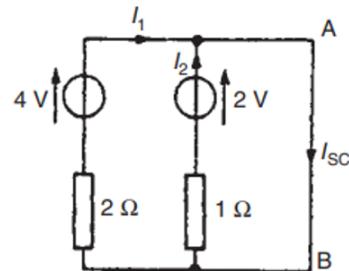


$$I_{SC} = I_1 + I_2 = \frac{4}{2} + \frac{2}{1} = 4 \text{ A}$$

- If the sources of e.m.f. are removed the resistance is:

$$r = \frac{2 \times 1}{2 + 1} = \frac{2}{3} \Omega$$


- From the Norton equivalent network

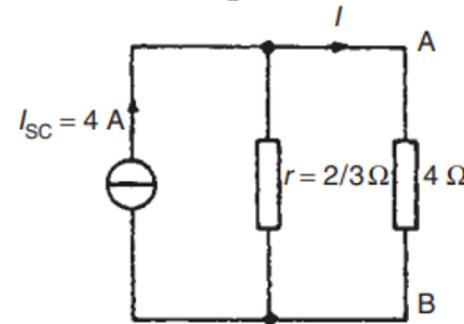

$$I = \left(\frac{\frac{2}{3}}{\frac{2}{3} + 4} \right) (4) = 0.571 \text{ A}$$

Maximum power transfer theorem

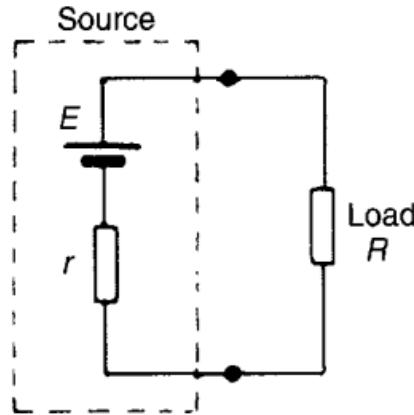
- *The power transferred from a supply source to a load is at its maximum when the resistance of the load is equal to the internal resistance of the source.*
- Hence, when $R = r$ the power transferred from the source to the load is a maximum.



- Applications of the maximum power transfer theorem are found in
 - i. Stereo amplifier design, seeking to maximise power delivered to speakers,
 - ii. Electric vehicle design, seeking to maximise power delivered to drive a motor

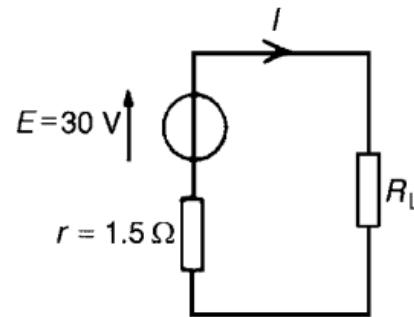Example

- A DC source has an open-circuit voltage of 30V and an internal resistance of 1.5Ω . State the value of load resistance that gives maximum power dissipation and determine the value of this power.



- For maximum power dissipation, $R_L = r = 1.5 \Omega$.


$$I = \frac{E}{(r + R_L)} = \frac{30}{(1.5 + 1.5)} = 10 \text{ A}$$

- Maximum power dissipated,


$$P = I^2 R_L = (10^2)(1.5) = 150 \text{ W}$$

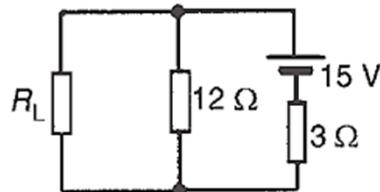Example

- Find the value of the load resistor R_L that gives maximum power dissipation and determine the value of this power.




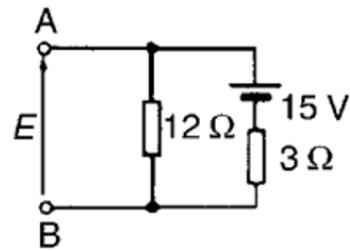- Resistance R_L is removed from the circuit




$$E = \left(\frac{12}{12 + 3} \right) (15) = 12V$$

- Removing the source of e.m.f.

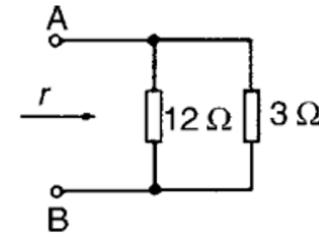

$$r = \frac{12 \times 3}{12 + 3} = 2.4 \Omega$$

- Thévenin's circuit

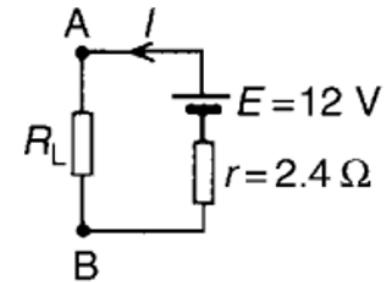

$$I = \frac{12}{2.4 + 2.4} = 2.5A$$

$$P = I^2 R_L = 2.5^2 (2.4) = 15 W$$



End of session



Questions....?