



# DIGITAL ELECTRONICS

## CHAPTER THREE: \*Simplification of Boolean Expressions Examples

By J. Mathenge


## 3.1 Simplification of Boolean Expressions

### Introduction:

- Given the below Boolean function to implement:

$$x = AB (\overline{A} + BC)$$

- It can be implemented as below:

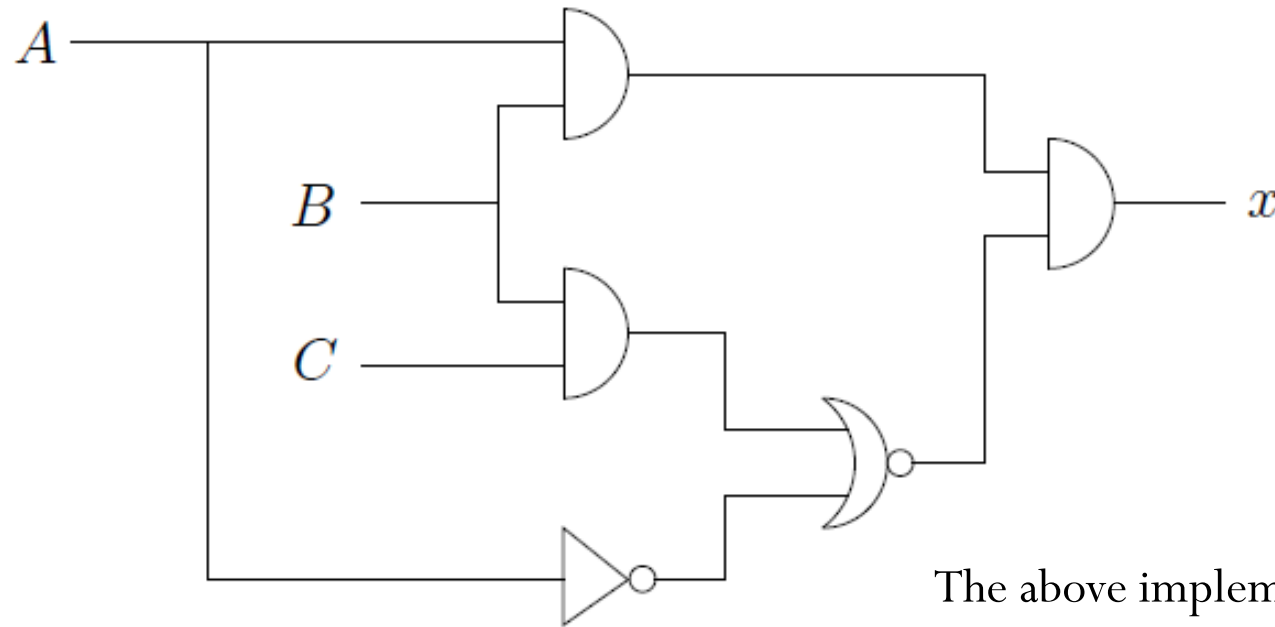

The above implementation requires 5 logic gates.

## 3.1 Simplification of Boolean Expression

- Suppose now we decided to simplify the expression before implementing it. From:

$$x = AB (\overline{\overline{A} + BC})$$

i. Using De Morgan's theorems we get:

$$x = AB (\overline{\overline{A}} \cdot \overline{BC})$$

$$\overline{\overline{A} + BC} = \overline{\overline{A}} \cdot \overline{BC}$$



1:	$A + B = B + A$
2:	$A + (B + C) = (A + B) + C$
3:	$A + B \cdot C = (A + B) \cdot (A + C)$
4:	$A + A \cdot B = A$
5:	$A + \overline{A} \cdot B = A + B$
6:	$A \cdot B + A \cdot \overline{B} = A$
7:	$A \cdot B + \overline{A} \cdot C = (A + C) \cdot (\overline{A} + B)$
8:	$A \cdot B + \overline{A} \cdot C + B \cdot C = A \cdot B + \overline{A} \cdot C$
9:	$\overline{A + B + C + \dots} = \overline{A} \cdot \overline{B} \cdot \overline{C} \dots$

$A \cdot B = B \cdot A$
$A \cdot (B \cdot C) = (A \cdot B) \cdot C$
$A \cdot (B + C) = A \cdot B + A \cdot C$
$A \cdot (A + B) = A$
$A \cdot (\overline{A} + B) = A \cdot B$
$(A + B) \cdot (A + \overline{B}) = A$
$(A + B) \cdot (\overline{A} + C) = A \cdot C + \overline{A} \cdot B$
$(A + B) \cdot (\overline{A} + C) \cdot (B + C) = (A + B) \cdot (\overline{A} + C)$
$\overline{A \cdot B \cdot C \dots} = \overline{A} + \overline{B} + \overline{C} + \dots$

## 3.1 Simplification of Boolean Expression

ii. Simplifying further we get:

$$= AB (A(\overline{B} + \overline{C}))$$

$$\overline{BC} = \overline{B} + \overline{C}$$



Opening the brackets

$$= AB (A\overline{B} + A\overline{C})$$


$$= AB A\overline{B} + AB A\overline{C}$$

Since  $B\overline{B} = 0$  and  $AA=A$



$$= AB\overline{C}$$

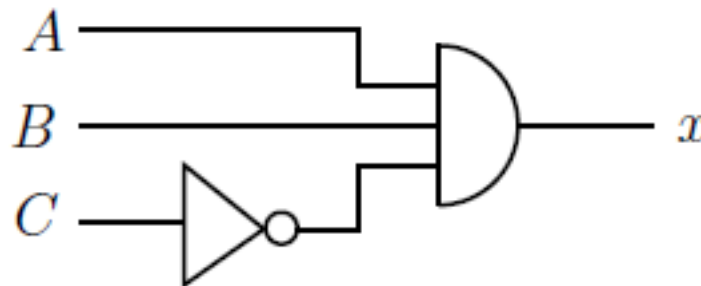- The simplified circuit can now be implemented using two gates as below:



## 3.1 Simplification of Boolean Expression

- The previous example shows it is necessary to reduce Boolean expressions before implementing them as it makes the final circuit:
  - i. **Cheaper** - less gates used, needs a smaller circuit board.
  - ii. More **reliable** as there are **fewer interconnections**.
  - iii. Have a **lower power consumption**.
- There are two methods of simplifying logic expressions:
  - i. **Algebraic** Simplification - Uses theorems of Boolean Algebra.
  - ii. The **Karnaugh map** method - Graphical.

### 3.1.1 Algebraic Simplification

- To use this method, you need to know the theorems of Boolean algebra very well.
- You shall need a lot of **practice** to build your skills for Algebraic Simplification.
- Generally, there are two steps when using this method:
  - I. Put the expression in **Sum of Products** form (*not* Product of Sums form). This may require the use of De Morgan's theorem or the distributive rules.
  - II. Check for **common factors** and **factor out** whenever possible. Factoring usually results in the elimination of some of the terms.

## Example 1 (Approach I)

Simplify algebraically:

$$ABC + AB\bar{C} + A\bar{B}C$$

- Since the expression is already in SOP form, so we shall just factor out the common terms:

$$AB\{C + \bar{C}\} + A\bar{B}C$$

- But,  $AB + A\bar{B}C = A\{B + \bar{B}C\}$
- Hence we have,  $A\{B + \bar{B}C\}$
- This reduces to  $A\{B + C\}$
- Opening the brackets we get:  $AB + AC$

Using the theorems

$$C + \bar{C} = 1$$

5:  $A + \bar{A} \cdot B = A + B$

6:  $A \cdot B + A \cdot \bar{B} = A$

## Example 1 (Approach II)

Simplify algebraically:

$$ABC + AB\bar{C} + A\bar{B}C$$

- Since the expression is already in SOP form, so we shall just factor out the common terms:

$$A\{BC + B\bar{C} + \bar{B}C\}$$

- But,  $BC + B\bar{C} = B$
- Hence we have,  $A\{B + \bar{B}C\}$
- This reduces to  $A\{B + C\}$
- Opening the brackets we get:  $AB + AC$

Using the theorems

$$\begin{array}{ll} 5: & A + \bar{A} \cdot B = A + B \\ 6: & A \cdot B + A \cdot \bar{B} = A \end{array}$$



## Example 2

**Simplify  $ABC + ABC' + AB'C + A'BC$**

Since the expression is in the SOP we proceed to factor out common terms:

$$AB\{C + C'\} + AB'C + A'BC$$

$$AB\{1\} + AB'C + A'BC$$

$$AB + AB'C + A'BC$$

$$B(A + A'C) + AB'C$$

$$B\{A + C\} + AB'C$$

$$AB + BC + AB'C$$

$$A\{B + B'C\} + BC$$

$$A\{B + C\} + BC$$

$$AB + AC + BC$$

Using the theorems

$$C + \bar{C} = 1$$

## Example 3

- Show that

$$ABC + ABC' + AB'C + A'BC = AB + AC + BC$$

It is easier to prove the RHS of the expression.

$$AB + AC + BC$$

We note that this is in SOP form. We now need to express it in the Standard SOP for it to match the expression on the right.

$$AB\{C + C'\} + AC\{B + B'\} + BC\{A + A'\}$$

$$ABC + ABC' + ABC + AB'C + ABC + A'BC$$

$$ABC + ABC' + AB'C + A'BC$$

The RHS=LHS hence proved.

## Example 4

Simplify the expression:

$$ABC + AB'C + A'BC + A'B'C + A'B'C'$$

Solution:

$$AC\{B + B'\} + A'C\{B + B'\} + A'B'C'$$

$$AC\{1\} + A'C\{1\} + A'B'C'$$

$$AC + A'C + A'B'C'$$

$$C\{A + A'\} + A'B'C'$$

$$C\{1\} + A'B'C'$$

$$C + A'B'C'$$

$$C + A'B'$$

Using the theorems

$$5: \quad A + \overline{A} \cdot B = A + B$$

$$6: \quad A \cdot B + A \cdot \overline{B} = A$$

## Example 5

Simplify  $x = ABC + (\overline{A} + \overline{B})(\overline{\overline{A}} + \overline{\overline{C}})$

$$X = ABC + (A' + B')(A'' + C'')$$

Since  $A'' = A$  and  $C'' = C$

The expression becomes:

$$X = ABC + (A' + B')(A + C)$$

Opening the brackets so that we have the SOP form

$$X = ABC + A'A + A'C + B'A + B'C$$

But  $A'A = 0$

$$\text{Hence } X = ABC + A'C + B'A + B'C$$

$$X = C(AB + A') + B'A + B'C$$

$$X = C(A' + B) + B'A + B'C$$

$$X = CA' + CB + B'A + B'C$$

$$X = CA' + B'A + C\{B + B'\} = CA' + B'A + C$$

$$X = C\{A' + 1\} + B'A = C + B'A$$

Using the theorems

5:  $A + \overline{A} \cdot B = A + B$

6:  $A \cdot B + A \cdot \overline{B} = A$

## Example 6

- A student may register for course X only if he satisfies the following conditions:
- (1) Has completed at least 20 courses AND is a Computing student AND of good conduct, OR
- (2) Has completed at least 20 courses AND is a Computing student AND has departmental approval, OR
- (3) Has completed fewer than 20 courses AND is a Computing student AND not of good conduct, OR
- (4) Is of good conduct AND has departmental approval, OR
- (5) Is a Computing student AND does not have departmental approval.

## Solution

Let the listed conditions be represented by the letters below:

- A: Has completed at least 20 courses
- B: Is a Computing student
- C: Is of good conduct
- D: Has departmental approval
- Y: Student may register for course X

$$Y = ABC + ABD + A'BC' + CD + BD'$$

We can now simplify this expression.

# Solution

$$Y = ABC + ABD + A'BC' + CD + BD'$$

$$Y = ABC + A'BC' + CD + B\{D' + DA\}$$

$$Y = ABC + A'BC' + CD + B\{D' + A\}$$

$$Y = ABC + A'BC' + CD + BD' + BA$$

$$Y = AB\{C + 1\} + A'BC' + CD + BD'$$

$$Y = AB + A'BC' + CD + BD'$$

$$Y = B\{A + A'C'\} + CD + BD'$$

$$Y = B\{A + C'\} + CD + BD'$$

$$Y = AB + BC' + CD + BD' \quad \text{*Rewrite } DC + D'B \text{ to match theorem \#8}$$

$$Y = AB + BC' + DC + D'B + CB = AB + BC' + CD + BD' + CB$$

$$Y = AB + B\{C' + C\} + CD + BD' = AB + B + CD + BD' = B(A + 1) + CD + BD'$$

$$Y = B + CD + BD' = B\{D' + 1\} + CD = \mathbf{B + CD}$$

Hence a student may register for the course X if he is a Computing student OR he is of good conduct AND has departmental approval.

Using the theorems

$$5: \quad A + \overline{A} \cdot B = A + B$$

$$6: \quad A \cdot B + A \cdot \overline{B} = A$$

$$8: \quad A \cdot B + \overline{A} \cdot C + B \cdot C = A \cdot B + \overline{A} \cdot C$$



*\*End of session\**





Questions....?